

Combinational Circuit Design

1.

```
module circuit (
    input [2:0] D,          // 3-bit input D
    input A, B, C, sel,    // Additional inputs
    output out, out_bar    // Outputs
);
    wire and_out, or_out, xnor_out, mux_out;

    assign and_out = D[0] & D[1]; // AND gate
    assign or_out = and_out | D[2]; // OR gate
    assign xnor_out = ~(A ^ B ^ C); // XNOR gate

    assign mux_out = sel ? xnor_out : or_out; // 2:1 MUX
    assign out = mux_out;
    assign out_bar = ~mux_out; // NOT gate

endmodule

module circuit_tb;

    reg [2:0] D;
    reg A, B, C, sel;
    wire out, out_bar;

    // Instantiate the module
    circuit uut (
        .D(D),
        .A(A),
        .B(B),
        .C(C),
        .sel(sel),
        .out(out),
        .out_bar(out_bar)
    );

    initial begin

        // Initialize inputs
        D = 3'b000;
        A = 0;
        B = 0;
        C = 0;
        sel = 0;

        #10; // Wait 10 time units before applying test cases
    end
endmodule
```


```

// Apply randomized test cases
repeat (10) begin
    D = $random;
    A = $random;
    B = $random;
    C = $random;
    sel = $random;
    #10;
end

$finish;
end

endmodule

```

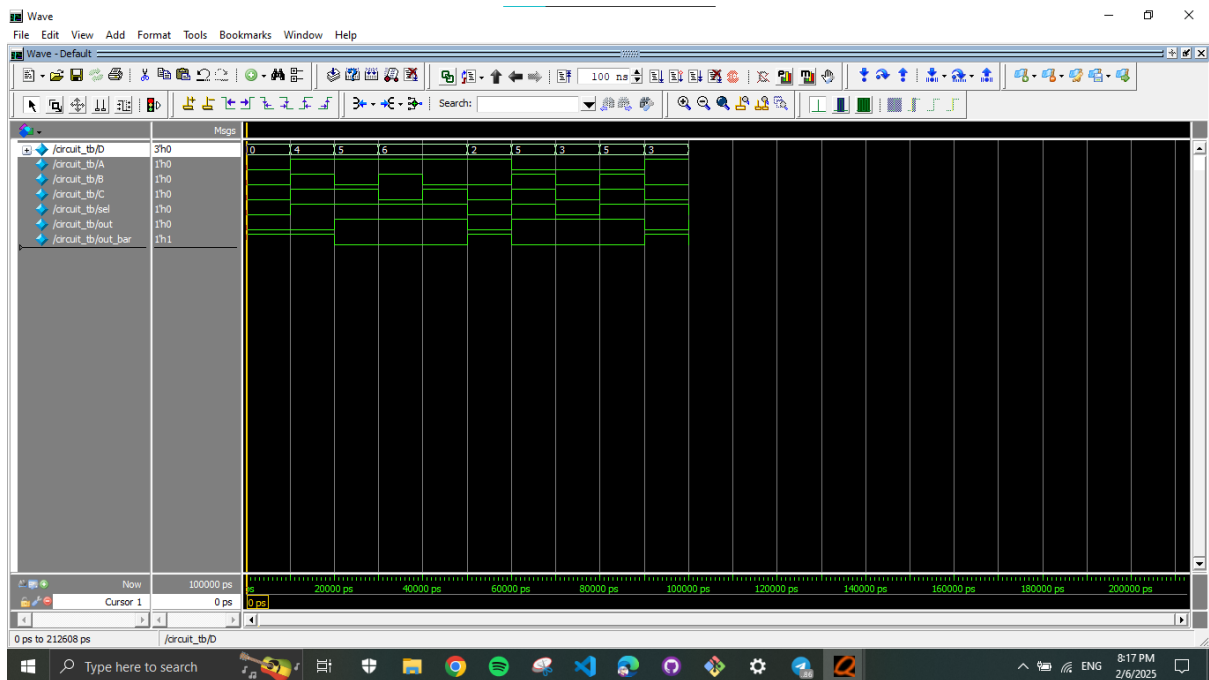

2.


```
module priority_encoder (  
    input [3:0] x, // 4-bit input  
    output reg [1:0] y // 2-bit output  
);  
    always @(*) begin  
  
        //Switch Cases  
        casex (x)  
            4'b1xxx: y = 2'b11; // Highest priority: x3 = 1  
            4'b01xx: y = 2'b10; // Second priority: x2 = 1  
            4'b001x: y = 2'b01; // Third priority: x1 = 1  
            default: y = 2'b00;  
        endcase  
  
        /*  
        //If-else  
        if (x[3] == 1'b1) y = 2'b11;  
        else if (x[2] == 1'b1) y = 2'b10;  
        else if (x[1] == 1'b1) y = 2'b01;  
        else y = 2'b00;  
        */  
  
    end  
endmodule  
  
module priority_encoder_tb;  
  
    reg [3:0] x;  
    wire [1:0] y;  
    reg [1:0] expected_y;  
  
    // Instantiate the module  
    priority_encoder uut (  
        .x(x),  
        .y(y)  
    );  
  
    initial begin  
  
        // Randomized test cases  
        repeat (10) begin  
            x = $random;  
            casex (x)  
                4'b1xxx: expected_y = 2'b11;  
                4'b01xx: expected_y = 2'b10;  
                4'b001x: expected_y = 2'b01;  
            endcase  
        end  
    end  
endmodule
```

```

        default: expected_y = 2'b00;
    endcase
    #10;
    check_output();
end
$finish;
end

// Task to check output
task check_output;
    if (y !== expected_y)
        $display("Test Failed: x = %b, Expected y = %b, Got y = %b", x,
expected_y, y);
    else
        $display("Test Passed: x = %b, y = %b", x, y);
    endtask
endmodule

```

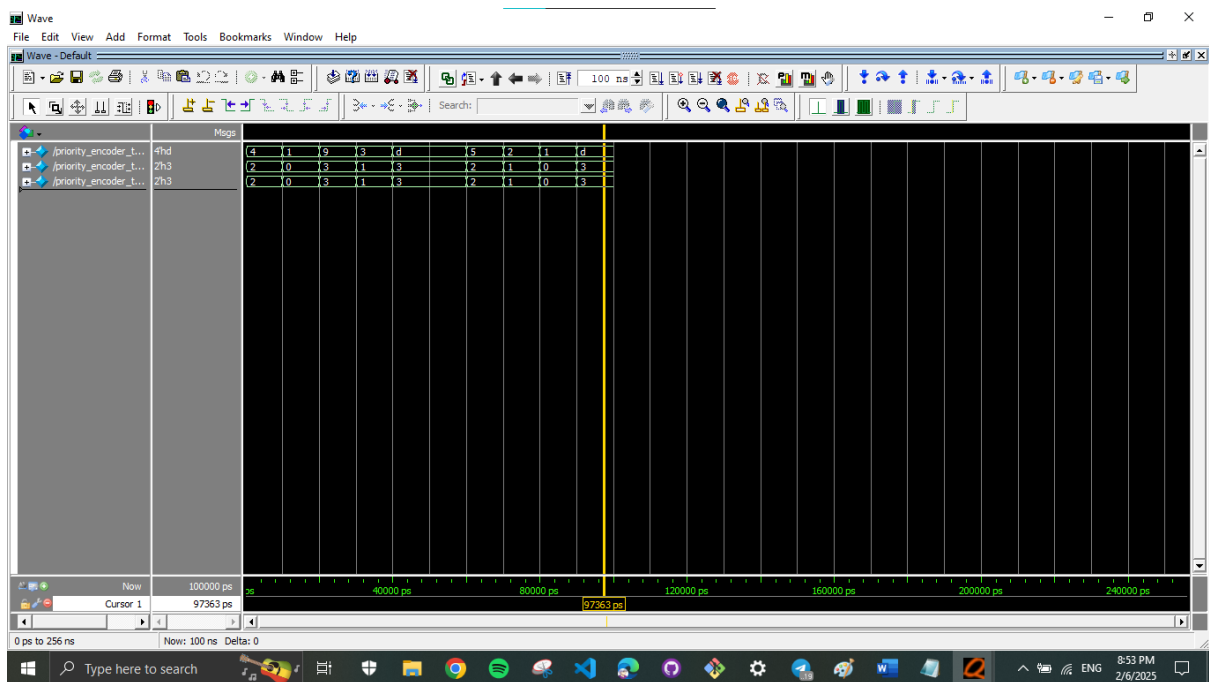

```

# Test Passed: x = 0100, y = 10
# Test Passed: x = 0001, y = 00
# Test Passed: x = 1001, y = 11
# Test Passed: x = 0011, y = 01
# Test Passed: x = 1101, y = 11
# Test Passed: x = 1101, y = 11
# Test Passed: x = 0101, y = 10
# Test Passed: x = 0010, y = 01
# Test Passed: x = 0001, y = 00
# Test Passed: x = 1101, y = 11

```

3.

```
module decimal_to_bcd_encoder (
    input  [9:0] d,      // 10-bit input (D0 to D9)
    output reg [3:0] y   // 4-bit output (Y3 to Y0)
);
    always @(*) begin
        case (d)
            10'b0000000001: y = 4'b0000; // 0
            10'b0000000010: y = 4'b0001; // 1
            10'b00000000100: y = 4'b0010; // 2
            10'b00000001000: y = 4'b0011; // 3
            10'b00000010000: y = 4'b0100; // 4
            10'b00000100000: y = 4'b0101; // 5
            10'b00001000000: y = 4'b0110; // 6
            10'b00010000000: y = 4'b0111; // 7
            10'b00100000000: y = 4'b1000; // 8
            10'b10000000000: y = 4'b1001; // 9
            default:        y = 4'b0000; // Default case (held zero)
        endcase
    end
endmodule

module decimal_to_bcd_encoder_tb;

    reg [9:0] d;
    wire [3:0] y;
    reg [3:0] expected_y;

    // Instantiate the module
    decimal_to_bcd_encoder uut (
        .d(d),
        .y(y)
    );

    initial begin

        // Test cases
        d = 10'b0000000001; expected_y = 4'b0000; #10; check_output(); //
0
        d = 10'b0000000010; expected_y = 4'b0001; #10; check_output(); //
1
        d = 10'b00000000100; expected_y = 4'b0010; #10; check_output(); //
2
        d = 10'b00000001000; expected_y = 4'b0011; #10; check_output(); //
3
    end
endmodule
```

```

4      d = 10'b0000010000; expected_y = 4'b0100; #10; check_output(); //
5      d = 10'b0000100000; expected_y = 4'b0101; #10; check_output(); //
6      d = 10'b0001000000; expected_y = 4'b0110; #10; check_output(); //
7      d = 10'b0010000000; expected_y = 4'b0111; #10; check_output(); //
8      d = 10'b0100000000; expected_y = 4'b1000; #10; check_output(); //
9      d = 10'b1000000000; expected_y = 4'b1001; #10; check_output(); //

// Invalid inputs (should return 0000)
d = 10'b0000000000; expected_y = 4'b0000; #10; check_output();
d = 10'b1111111111; expected_y = 4'b0000; #10; check_output();
d = 10'b0000000011; expected_y = 4'b0000; #10; check_output();

// Randomized tests
repeat (5) begin
    d = 1 << ($random % 10); // Generate random valid input
    casex (d)
        10'b0000000001: expected_y = 4'b0000;
        10'b0000000010: expected_y = 4'b0001;
        10'b0000000100: expected_y = 4'b0010;
        10'b0000001000: expected_y = 4'b0011;
        10'b0000010000: expected_y = 4'b0100;
        10'b0000100000: expected_y = 4'b0101;
        10'b0001000000: expected_y = 4'b0110;
        10'b0010000000: expected_y = 4'b0111;
        10'b0100000000: expected_y = 4'b1000;
        10'b1000000000: expected_y = 4'b1001;
        default: expected_y = 4'b0000;
    endcase
    #10;
    check_output();
end


$stop;
end

// Task to check output
task check_output;
    if (y !== expected_y)
        $display("Test Failed: d = %b, Expected y = %b, Got y = %b",
d, expected_y, y);
    else
        $display("Test Passed: d = %b, y = %b", d, y);

```

endtask


endmodule

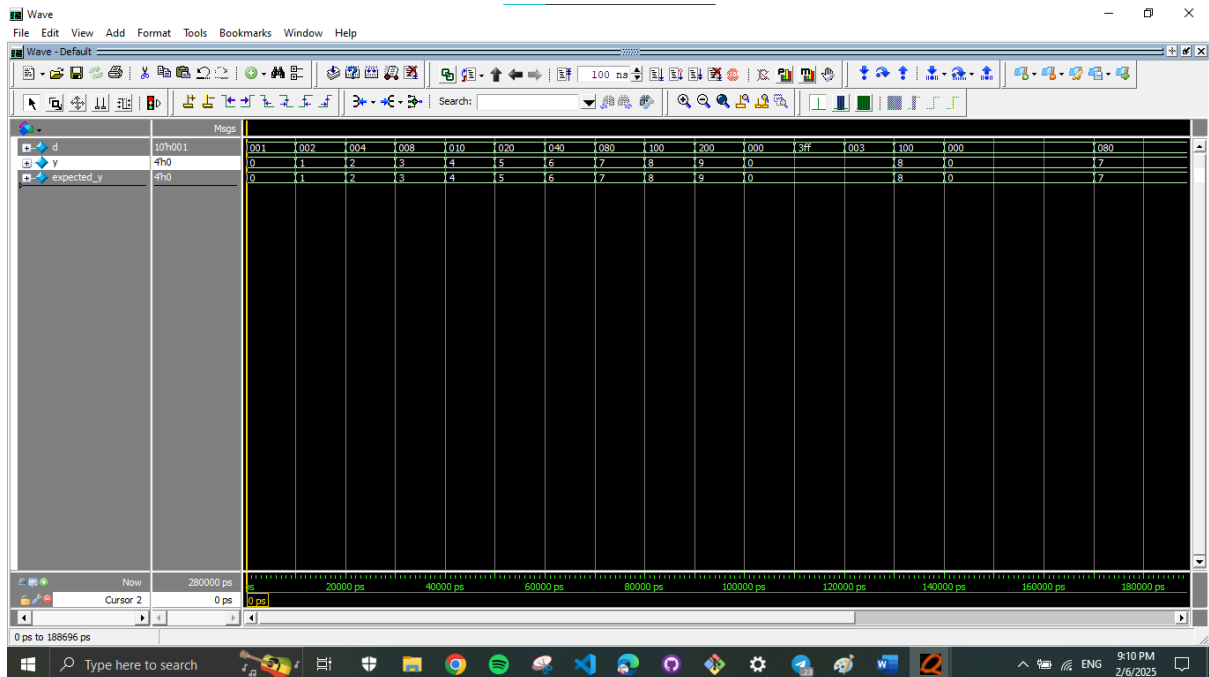

```
# Test Passed: d = 0000000001, y = 0000
# Test Passed: d = 0000000010, y = 0001
# Test Passed: d = 0000000100, y = 0010
# Test Passed: d = 0000001000, y = 0011
# Test Passed: d = 0000010000, y = 0100
# Test Passed: d = 0000100000, y = 0101
# Test Passed: d = 0001000000, y = 0110
# Test Passed: d = 0010000000, y = 0111
# Test Passed: d = 0100000000, y = 1000
# Test Passed: d = 1000000000, y = 1001
# Test Passed: d = 0000000000, y = 0000
# Test Passed: d = 1111111111, y = 0000
# Test Passed: d = 0000000011, y = 0000
# Test Passed: d = 0100000000, y = 1000
# Test Passed: d = 0000000000, y = 0000
# Test Passed: d = 0000000000, y = 0000
# Test Passed: d = 0000000000, y = 0000
# Test Passed: d = 0010000000, y = 0111
```

 
4.

```
module Nbit_adder #(parameter N = 1) (  
    input [N-1:0] A,  
    input [N-1:0] B,  
    output [N-1:0] C  
);  
    assign C = A + B; // Dataflow modeling  
endmodule  
  
module Nbit_adder_tb;  
    parameter N = 4; // Example with 4 bits  
    reg [N-1:0] A, B;  
    wire [N-1:0] C;  
    reg [N-1:0] expected_result;  
  
    // Instantiate the adder  
    Nbit_adder #(N) adder (  
        .A(A),  
        .B(B),  
        .C(C)  
    );  
  
    initial begin  
        // Randomize inputs and check the result  
        repeat (10) begin  
            A = $random;  
            B = $random;  
            expected_result = A + B;  
  
            #10;  
            check_output;  
        end  
  
        $finish;  
    end  
  
    // Task to check output  
    task check_output;  
        if (C !== expected_result)  
            $display("Test failed: A = %b, B = %b, C = %b, Expected = %b",  
A, B, C, expected_result);  
        else  
            $display("Test passed: A = %b, B = %b, C = %b", A, B, C);  
        endtask  
    endmodule
```



```
# Test passed: A = 0100, B = 0001, C = 0101
# Test passed: A = 1001, B = 0011, C = 1100
# Test passed: A = 1101, B = 1101, C = 1010
# Test passed: A = 0101, B = 0010, C = 0111
# Test passed: A = 0001, B = 1101, C = 1110
# Test passed: A = 0110, B = 1101, C = 0011
# Test passed: A = 1101, B = 1100, C = 1001
# Test passed: A = 1001, B = 0110, C = 1111
# Test passed: A = 0101, B = 1010, C = 1111
# Test passed: A = 0101, B = 0111, C = 1100
```

5.

```
module Nbit_ALU #(parameter N = 4) (
    input [N-1:0] A,
    input [N-1:0] B,
    input [1:0] opcode,
    output reg [N-1:0] result
);
    wire [N-1:0] add_result;

    // Instantiate the adder for addition
    Nbit_adder #(N) adder (
        .A(A),
        .B(B),
        .C(add_result)
    );

    always @(*) begin
        case (opcode)
            2'b00: result = add_result; // Addition
            2'b01: result = A - B; // Subtraction
            2'b10: result = A | B; // OR
            2'b11: result = A ^ B; // XOR
            default: result = {N{1'b0}}; // Default case
        endcase
    end
endmodule

module Nbit_ALU_tb;
    parameter N = 4;
    reg [N-1:0] A, B;
    reg [1:0] opcode;
    wire [N-1:0] result;
    reg [N-1:0] expected_result;

    // Instantiate the ALU
    Nbit_ALU #(N) alu (
        .A(A),
        .B(B),
        .opcode(opcode),
        .result(result)
    );

    // Task for checking the result
    task check_result;
        input [N-1:0] expected;
        begin
            if (result !== expected) begin
```

```

        $display("Test failed: A = %b, B = %b, opcode = %b, result
= %b, Expected = %b", A, B, opcode, result, expected);
    end else begin
        $display("Test passed: A = %b, B = %b, opcode = %b, result
= %b", A, B, opcode, result);
    end
end
endtask

initial begin
    // Randomize inputs and check the result
    repeat (10) begin
        A = $random;
        B = $random;
        opcode = $random % 4; // Random opcode between 0 and 3


        case (opcode)
            2'b00: expected_result = A + B;    // Addition
            2'b01: expected_result = A - B;    // Subtraction
            2'b10: expected_result = A | B;    // OR
            2'b11: expected_result = A ^ B;    // XOR
        endcase

        #10; // Wait for the result

        // Call the check_result task
        check_result(expected_result);
    end

    $finish;
end
endmodule

```

 

```
# Test passed: A = 0100, B = 0001, opcode = 01, result = 0011
# Test passed: A = 0011, B = 1101, opcode = 01, result = 0110
# Test passed: A = 0101, B = 0010, opcode = 01, result = 0011
# Test passed: A = 1101, B = 0110, opcode = 01, result = 0111
# Test passed: A = 1101, B = 1100, opcode = 01, result = 0001
# Test passed: A = 0110, B = 0101, opcode = 10, result = 0111
# Test passed: A = 0101, B = 0111, opcode = 10, result = 0111
# Test passed: A = 1111, B = 0010, opcode = 10, result = 1111
# Test passed: A = 1000, B = 0101, opcode = 00, result = 1101
# Test passed: A = 1101, B = 1101, opcode = 01, result = 0000
```

6.

```
module ALU_7seg_display (
    input [3:0] A,
    input [3:0] B,
    input [1:0] opcode,
    input enable,
    output reg [6:0] seg // a-g
);
    wire [3:0] alu_result;

    // Instantiate the 4-bit ALU
    Nbit_ALU #(4) alu (
        .A(A),
        .B(B),
        .opcode(opcode),
        .result(alu_result)
    );

    // 7-segment decoder
    always @(*) begin
        if (enable) begin
            case (alu_result)
                4'h0: seg = 7'b1111110;
                4'h1: seg = 7'b0110000;
                4'h2: seg = 7'b1101101;
                4'h3: seg = 7'b1111001;
                4'h4: seg = 7'b0110011;
                4'h5: seg = 7'b1011011;
                4'h6: seg = 7'b1011111;
                4'h7: seg = 7'b1110000;
                4'h8: seg = 7'b1111111;
                4'h9: seg = 7'b1111011;
                4'hA: seg = 7'b1110111;
                4'hB: seg = 7'b0011111;
                4'hC: seg = 7'b1001110;
                4'hD: seg = 7'b0111101;
                4'hE: seg = 7'b1001111;
                4'hF: seg = 7'b1000111;
                default: seg = 7'b0000000;
            endcase
        end else begin
            seg = 7'b0000000; // Display off
        end
    end
endmodule
```

```

module ALU_7seg_display_tb;
    reg [3:0] A, B;
    reg [1:0] opcode;
    reg enable;
    wire [6:0] seg;
    reg [6:0] expected_seg;

    // Instantiate the ALU with 7-segment display
    ALU_7seg_display display (
        .A(A),
        .B(B),
        .opcode(opcode),
        .enable(enable),
        .seg(seg)
    );

    // Task for checking the result
    task check_result;
        input [6:0] expected;
        begin
            if (seg !== expected) begin
                $display("Test failed: A = %b, B = %b, opcode = %b, enable
= %b, seg = %b, Expected = %b", A, B, opcode, enable, seg, expected);
            end else begin
                $display("Test passed: A = %b, B = %b, opcode = %b, enable
= %b, seg = %b", A, B, opcode, enable, seg);
            end
        end
    endtask

    initial begin
        // Test vectors for all digits with enable = 1
        enable = 1;
        A = 4'h0; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1111110;
#10; check_result(expected_seg); // 0
        A = 4'h1; B = 4'h0; opcode = 2'b00; expected_seg = 7'b0110000;
#10; check_result(expected_seg); // 1
        A = 4'h2; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1101101;
#10; check_result(expected_seg); // 2
        A = 4'h3; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1111001;
#10; check_result(expected_seg); // 3
        A = 4'h4; B = 4'h0; opcode = 2'b00; expected_seg = 7'b0110011;
#10; check_result(expected_seg); // 4
        A = 4'h5; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1011011;
#10; check_result(expected_seg); // 5
        A = 4'h6; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1011111;
#10; check_result(expected_seg); // 6
    end

```

```


        A = 4'h7; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1110000;
#10; check_result(expected_seg); // 7
        A = 4'h8; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1111111;
#10; check_result(expected_seg); // 8
        A = 4'h9; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1111011;
#10; check_result(expected_seg); // 9
        A = 4'hA; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1110111;
#10; check_result(expected_seg); // A
        A = 4'hB; B = 4'h0; opcode = 2'b00; expected_seg = 7'b0011111;
#10; check_result(expected_seg); // b
        A = 4'hC; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1001110;
#10; check_result(expected_seg); // C
        A = 4'hD; B = 4'h0; opcode = 2'b00; expected_seg = 7'b0111101;
#10; check_result(expected_seg); // d
        A = 4'hE; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1001111;
#10; check_result(expected_seg); // E
        A = 4'hF; B = 4'h0; opcode = 2'b00; expected_seg = 7'b1000111;
#10; check_result(expected_seg); // F

        // Test vector with enable = 0
        enable = 0;
        A = 4'h0; B = 4'h0; opcode = 2'b00; expected_seg = 7'b0000000;
#10; check_result(expected_seg); // Display off

    $finish;
end

endmodule

```

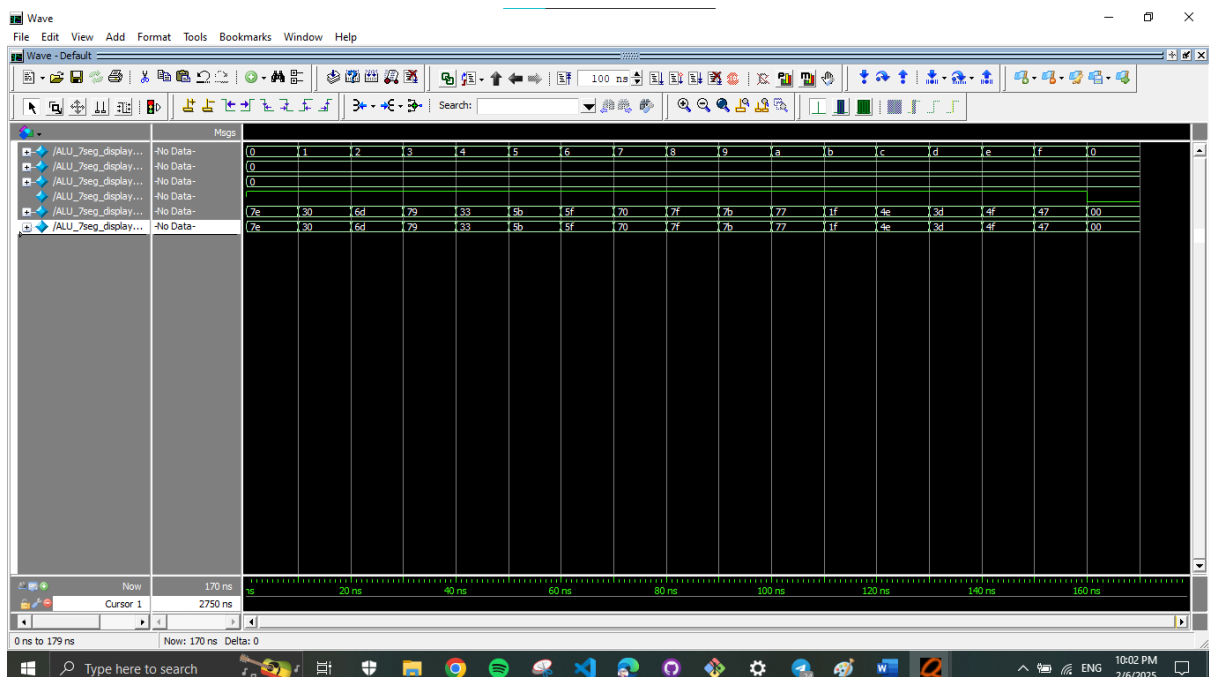


```
# Test passed: A = 0000, B = 0000, opcode = 00, enable = 1, seg = 1111110
# Test passed: A = 0001, B = 0000, opcode = 00, enable = 1, seg = 0110000
# Test passed: A = 0010, B = 0000, opcode = 00, enable = 1, seg = 1101101
# Test passed: A = 0011, B = 0000, opcode = 00, enable = 1, seg = 1111001
# Test passed: A = 0100, B = 0000, opcode = 00, enable = 1, seg = 0110011
# Test passed: A = 0101, B = 0000, opcode = 00, enable = 1, seg = 1011011
# Test passed: A = 0110, B = 0000, opcode = 00, enable = 1, seg = 1011111
# Test passed: A = 0111, B = 0000, opcode = 00, enable = 1, seg = 1110000
# Test passed: A = 1000, B = 0000, opcode = 00, enable = 1, seg = 1111111
# Test passed: A = 1001, B = 0000, opcode = 00, enable = 1, seg = 1111011
# Test passed: A = 1010, B = 0000, opcode = 00, enable = 1, seg = 1110111
# Test passed: A = 1011, B = 0000, opcode = 00, enable = 1, seg = 0011111
# Test passed: A = 1100, B = 0000, opcode = 00, enable = 1, seg = 1001110
# Test passed: A = 1101, B = 0000, opcode = 00, enable = 1, seg = 0111101
# Test passed: A = 1110, B = 0000, opcode = 00, enable = 1, seg = 1001111
# Test passed: A = 1111, B = 0000, opcode = 00, enable = 1, seg = 1000111
# Test passed: A = 0000, B = 0000, opcode = 00, enable = 0, seg = 0000000
```