

# Sequential Logic Design

1.


```
module D_latch (
    input wire D,    // Data Input
    input wire G,    // Enable (Gate)
    input wire CLR,  // Active Low Clear
    output reg Q     // Output
);
    always @(*) begin
        if (!CLR) begin    // Active low clear
            Q = 0;
        end else if (G) begin    // When G is high, latch follows D
            Q = D;
        end
        // When G is low, Q retains its value (latch behavior)
    end
endmodule

module D_latch_tb;
    reg D, G, CLR;
    wire Q;

    // Instantiate the data latch
    D_latch uut (
        .D(D),
        .G(G),
        .CLR(CLR),
        .Q(Q)
    );

    // Testbench logic
    initial begin
        // Randomized test sequence
        repeat (50) begin
            D = $random;
            G = $random;
            CLR = $random;
            #1; // Delay to avoid treating G as a clock
            $display("Time=%0t | CLR=%b, G=%b, D=%b | Q=%b", $time, CLR, G, D,
Q);
        end

         // End simulation
        $finish;
    end
endmodule
```



```
# Time=1 | CLR=1, G=1, D=0 | Q=0
# Time=2 | CLR=1, G=1, D=1 | Q=1
# Time=3 | CLR=1, G=0, D=1 | Q=1
# Time=4 | CLR=1, G=0, D=1 | Q=1
# Time=5 | CLR=1, G=0, D=1 | Q=1
# Time=6 | CLR=0, G=1, D=0 | Q=0
# Time=7 | CLR=0, G=1, D=1 | Q=0
# Time=8 | CLR=0, G=0, D=1 | Q=0
# Time=9 | CLR=0, G=1, D=0 | Q=0
# Time=10 | CLR=1, G=1, D=1 | Q=1
# Time=11 | CLR=0, G=0, D=1 | Q=0
# Time=12 | CLR=1, G=0, D=0 | Q=0
# Time=13 | CLR=1, G=1, D=0 | Q=0
# Time=14 | CLR=1, G=1, D=1 | Q=1
# Time=15 | CLR=1, G=0, D=0 | Q=1
# Time=16 | CLR=0, G=1, D=1 | Q=0
# Time=17 | CLR=0, G=0, D=0 | Q=0
# Time=18 | CLR=0, G=1, D=0 | Q=0
# Time=19 | CLR=1, G=1, D=0 | Q=0
# Time=20 | CLR=0, G=0, D=0 | Q=0
# Time=21 | CLR=1, G=0, D=0 | Q=0
# Time=22 | CLR=1, G=1, D=1 | Q=1
# Time=23 | CLR=0, G=0, D=1 | Q=0
# Time=24 | CLR=1, G=1, D=1 | Q=1
# Time=25 | CLR=1, G=0, D=0 | Q=1
# Time=26 | CLR=1, G=0, D=1 | Q=1
# Time=27 | CLR=1, G=0, D=1 | Q=1
# Time=28 | CLR=0, G=1, D=1 | Q=0
# Time=29 | CLR=0, G=1, D=1 | Q=0
# Time=30 | CLR=0, G=0, D=0 | Q=0
```

## 2. A.

```
module tff (  
    input wire t,           // Toggle input  
    input wire clk,         // Clock input  
    input wire rstn,        // Active low asynchronous reset  
    output reg q,           // Output  
    output wire qbar        // Complementary output  
);  
    assign qbar = ~q;  
  
    always @(posedge clk or negedge rstn) begin  
        if (!rstn)          // Active low reset  
            q <= 0;  
        else if (t)         // Toggle output when t = 1  
            q <= ~q;  
    end  
  
endmodule
```

## B.

```
module dff (  
    input wire d,           // Data input  
    input wire rstn,        // Active low asynchronous reset  
    input wire clk,         // Clock input  
    output reg q,           // Flip-Flop output  
    output wire qbar        // Complementary output (inverted q)  
);  
    assign qbar = ~q;       // Complementary output  
  
    always @(posedge clk or negedge rstn) begin  
        if (!rstn) begin    // Asynchronous reset (active low)  
            q <= 0;         // Reset output to 0  
        end else begin  
            q <= d;         // On clock edge, store input d  
        end  
    end  
  
endmodule
```

C.

```
module parameterized_ff
#(
    parameter FF_TYPE = "DFF" // Parameter to select flip-flop type: "DFF" or
                                "TFF"
)(
    input wire d,      // Data or toggle input
    input wire rstn,   // Active low reset
    input wire clk,    // Clock input
    output reg q,      // Output
    output wire qbar   // Complement of the output
);

    // qbar is always the complement of q
    assign qbar = ~q;

    // Always block triggered on the rising edge of clk or falling edge of
    rstn
    always @(posedge clk or negedge rstn) begin
        if (!rstn) begin
            // If reset is active (low), set q to 0
            q <= 0;
        end else begin
            if (FF_TYPE == "DFF") begin
                // D Flip-Flop behavior: q follows d
                q <= d;
            end else if (FF_TYPE == "TFF") begin
                // T Flip-Flop behavior: q toggles if d (toggle input) is 1
                q <= q ^ d;
            end
        end
    end
end

endmodule

/*
generate
    if (FF_TYPE == "DFF") begin : dff_inst
        dff dff_module (
            .d(d),
            .rstn(rstn),
            .clk(clk),
            .q(q),
            .qbar(qbar)
        );
    end else if (FF_TYPE == "TFF") begin : tff_inst
        tff tff_module (
            .t(d),      // 'd' acts as 't' in T Flip-Flop mode

```

```

        .rstn(rstn),
        .clk(clk),
        .q(q),
        .qbar(qbar)
    );
end
endgenerate
*/

```

## D. 1.

```

module param_ff_tb1;

    reg d, clk, rstn;
    wire q_param, qbar_param;
    wire q_golden, qbar_golden;

    // Instantiate parameterized Flip-Flop with DFF behavior
    param_ff #(.FF_TYPE("DFF")) uut (
        .d(d),
        .rstn(rstn),
        .clk(clk),
        .q(q_param),
        .qbar(qbar_param)
    );

    // Instantiate golden model (DFF)
    dff golden_model (
        .d(d),
        .rstn(rstn),
        .clk(clk),
        .q(q_golden),
        .qbar(qbar_golden)
    );

    // Clock Generation
    always #5 clk = ~clk; // Generate a 10ns clock period

    // Task to check correctness
    task check_output;
        if (q_param != q_golden || qbar_param != qbar_golden)
            $display("Mismatch at time %0t: q_param=%b, q_golden=%b", $time, q_param, q_golden);
        else
            $display("Pass at time %0t: q_param=%b, q_golden=%b", $time, q_param, q_golden);
    endtask

    initial begin
        // Initialize signals

```

```

    clk = 0;
    rstn = 0;
    d = 0;

    // Apply Reset
    #10 rstn = 1;


    // Apply test vectors using repeat loop
    repeat (20) begin
        #10 d = $random;
        #10 check_output;
    end

    // Apply reset and observe outputs
    #10 rstn = 0;
    #10 rstn = 1;
    check_output;

    // Finish simulation
    #50 $finish;
end

endmodule

```

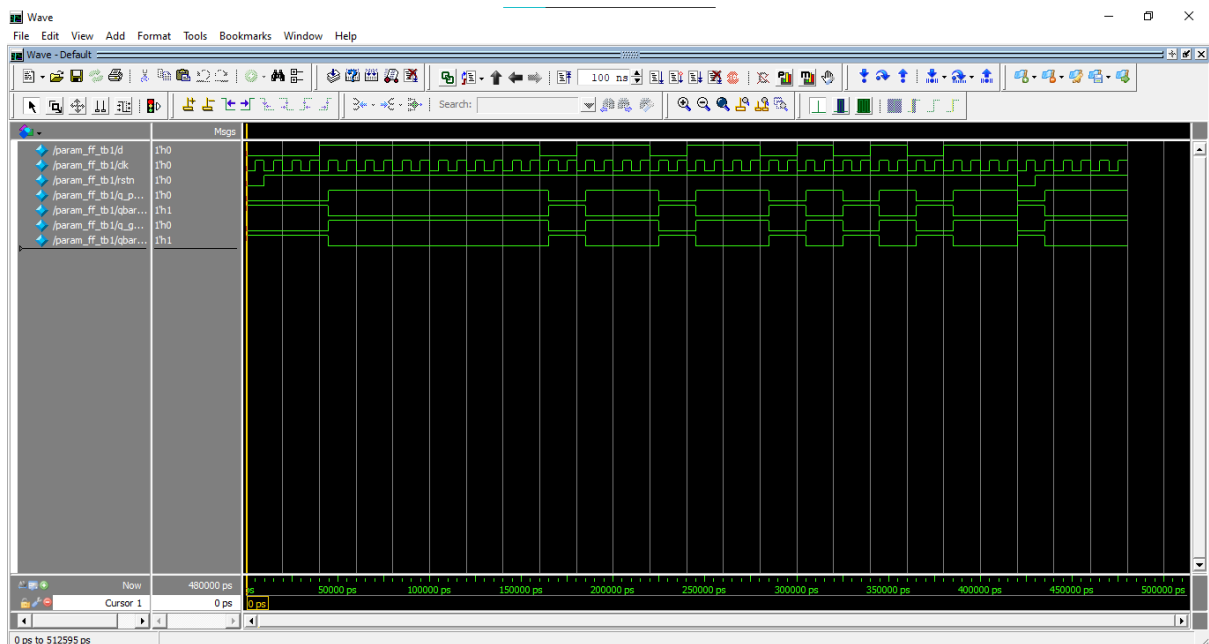

```

# Pass at time 30000: q_param=0, q_golden=0
# Pass at time 50000: q_param=1, q_golden=1
# Pass at time 70000: q_param=1, q_golden=1
# Pass at time 90000: q_param=1, q_golden=1
# Pass at time 110000: q_param=1, q_golden=1
# Pass at time 130000: q_param=1, q_golden=1
# Pass at time 150000: q_param=1, q_golden=1

```

```

# Pass at time 170000: q_param=0, q_golden=0
# Pass at time 190000: q_param=1, q_golden=1
# Pass at time 210000: q_param=1, q_golden=1
# Pass at time 230000: q_param=0, q_golden=0
# Pass at time 250000: q_param=1, q_golden=1
# Pass at time 270000: q_param=1, q_golden=1
# Pass at time 290000: q_param=0, q_golden=0
# Pass at time 310000: q_param=1, q_golden=1
# Pass at time 330000: q_param=0, q_golden=0
# Pass at time 350000: q_param=1, q_golden=1
# Pass at time 370000: q_param=0, q_golden=0
# Pass at time 390000: q_param=1, q_golden=1
# Pass at time 410000: q_param=1, q_golden=1
# Pass at time 430000: q_param=0, q_golden=0

```

## D. 2.

```

module param_ff_tb2;

    reg t, clk, rstn;
    wire q_param, qbar_param;
    wire q_golden, qbar_golden;

    // Instantiate parameterized Flip-Flop with TFF behavior
    param_ff #(.FF_TYPE("TFF")) uut (
        .d(t), // In TFF mode, d acts as t
        .rstn(rstn),
        .clk(clk),
        .q(q_param),
        .qbar(qbar_param)
    );

    // Instantiate golden model (TFF)
    tff golden_model (
        .t(t),
        .rstn(rstn),
        .clk(clk),
        .q(q_golden),
        .qbar(qbar_golden)
    );

    // Clock Generation
    always #5 clk = ~clk; // Generate a 10ns clock period
    // Task to check correctness
    task check_output;
        if (q_param !== q_golden || qbar_param !== qbar_golden)
            $display("Mismatch at time %0t: q_param=%b, q_golden=%b", $time, q_param, q_golden);
    endtask

```



```

else
    $display("Pass at time %0t: q_param=%b, q_golden=%b", $time, q_param, q_golden);
endtask

initial begin
    // Initialize signals
    clk = 0;
    rstn = 0;
    t = 0;

    // Apply Reset
    #10 rstn = 1;


    // Apply test vectors using repeat loop
    repeat (20) begin
        #10 t = 1; // Toggle
        #10 t = 0;
        check_output;
    end

    // Apply reset and observe outputs
    #10 rstn = 0;
    #10 rstn = 1;
    check_output;

    // Finish simulation
    #50 $finish;
end

endmodule

```

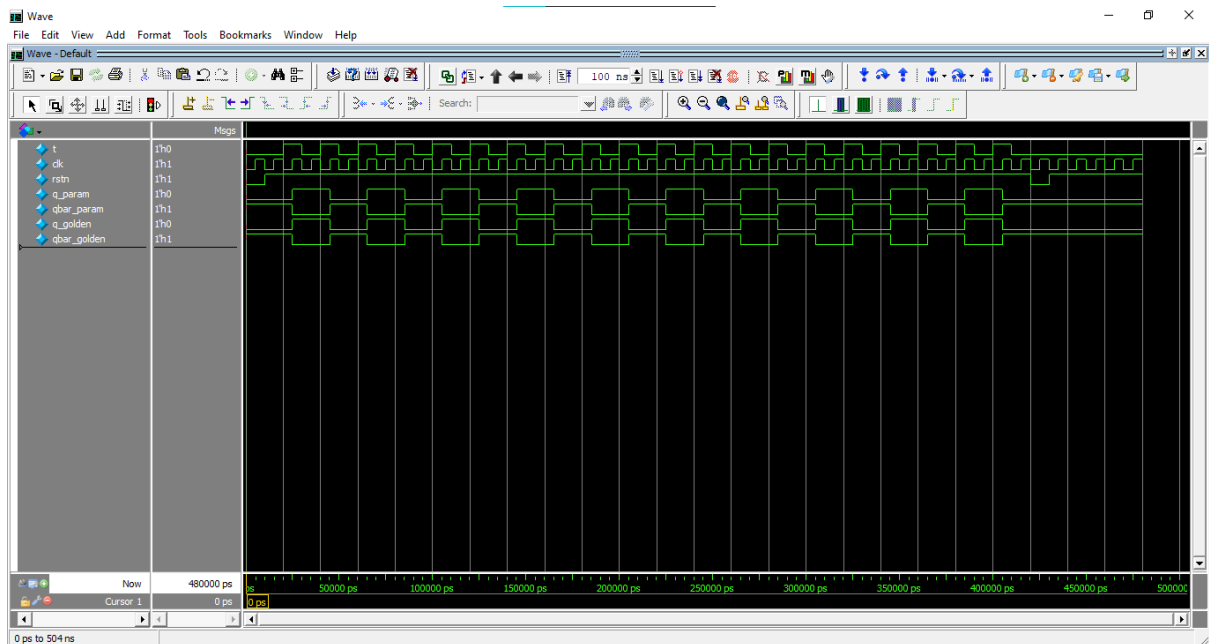

```
# Pass at time 30000: q_param=1, q_golden=1
# Pass at time 50000: q_param=0, q_golden=0
# Pass at time 70000: q_param=1, q_golden=1
# Pass at time 90000: q_param=0, q_golden=0
# Pass at time 110000: q_param=1, q_golden=1
# Pass at time 130000: q_param=0, q_golden=0
# Pass at time 150000: q_param=1, q_golden=1
# Pass at time 170000: q_param=0, q_golden=0
# Pass at time 190000: q_param=1, q_golden=1
# Pass at time 210000: q_param=0, q_golden=0
# Pass at time 230000: q_param=1, q_golden=1
# Pass at time 250000: q_param=0, q_golden=0
# Pass at time 270000: q_param=1, q_golden=1
# Pass at time 290000: q_param=0, q_golden=0
# Pass at time 310000: q_param=1, q_golden=1
# Pass at time 330000: q_param=0, q_golden=0
# Pass at time 350000: q_param=1, q_golden=1
# Pass at time 370000: q_param=0, q_golden=0
# Pass at time 390000: q_param=1, q_golden=1
# Pass at time 410000: q_param=0, q_golden=0
# Pass at time 430000: q_param=0, q_golden=0
```

```
// run.do
vlib wrok
```

```
# Compile Design and Testbenches
vlog param_FF.v
vlog D_FF.v
vlog T_FF.v
vlog param_FF_tb1.v
vlog param_FF_tb2.v
```

```
# Run Testbench 1 (DFF mode)
vsim -voptargs=+acc param_ff_tb1
add wave *
run -all
quit
```

```
# Run Testbench 2 (TFF mode)
vsim -voptargs=+acc param_FF_tb2
add wave *
run -all
quit
```

3.

```
module ripple_counter (
    input wire clk,    // Clock input
    input wire rstn,   // Active low reset
    output wire [3:0] out // 4-bit output
);

    // Internal signals for the flip-flop outputs
    wire [3:0] q;

    // Generate block to instantiate D flip-flops
    genvar i;
    generate
        for (i = 0; i < 4; i = i + 1) begin : gen_ff
            dff ff (
                .d(~q[i]), // Toggle input
                .rstn(rstn),
                .clk(i == 0 ? clk : q[i-1]), // First flip-flop, clocked by the main clock
                .q(q[i]),
                .qbar()
            );
        end
    endgenerate

    // Assign the outputs
    assign out = q;
endmodule

module ripple_counter_tb;

    // Declare testbench signals
    reg clk;
    reg rstn;
    wire [3:0] out;

    // Instantiate the 4-bit ripple counter
    ripple_counter uut (
        .clk(clk),
        .rstn(rstn),
        .out(out)
    );

    // Clock generation: 10 time unit period
    always begin
        #5 clk = ~clk; // Generate a clock with a period of 10 time units
    end
end
```

```

// Stimulus process: Generate randomized reset and check the output
initial begin
    // Initialize signals
    clk = 0;
    rstn = 0;

    // Apply reset
    #10 rstn = 1; // Assert reset after 10 time units

    // Randomize and test the counter's behavior
    #10 rstn = 0; // De-assert reset


    // Wait for a few clock cycles and then check the output
    #40;

    // Randomize the reset and observe the ripple counter
    repeat (10) begin
        #20 rstn = $random; // Randomize reset signal
        #10; // Wait for a clock cycle
    end

    // End simulation after 200 time units
    #200;
    $stop;
end

// Monitor the outputs to check correctness
initial begin
    $monitor("At time %t: out = %b", $time, out);
end
endmodule

```

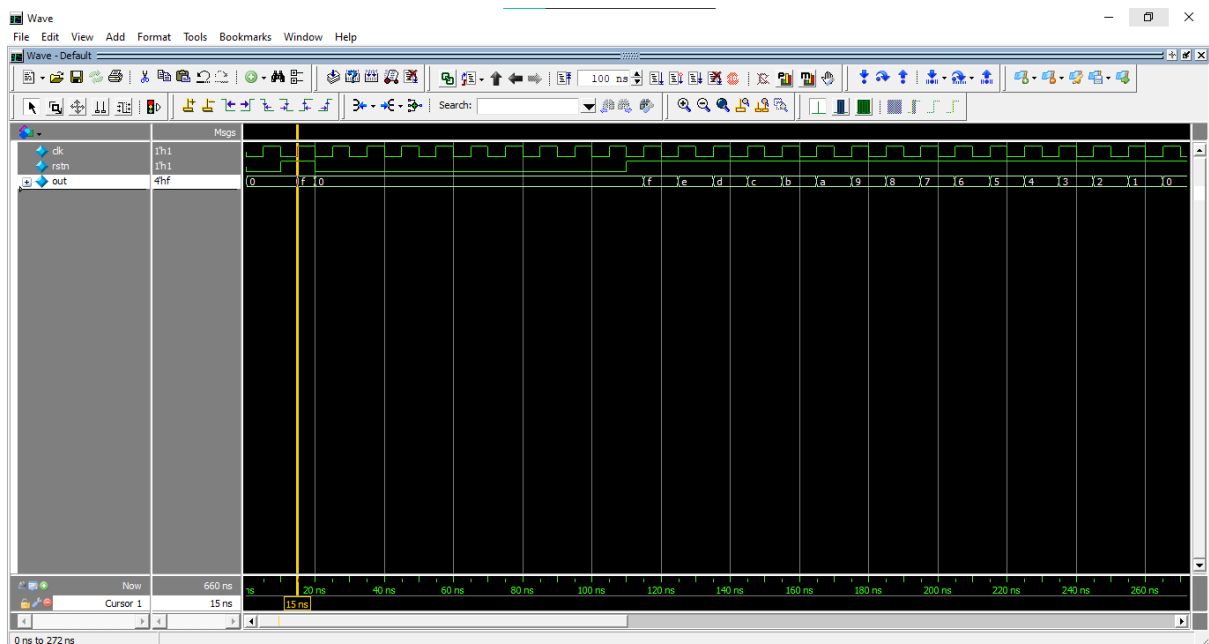

4.

```
module param_shift_register #(
    parameter LOAD_AVALUE = 1,
    parameter LOAD_SVALUE = 1,
    parameter SHIFT_WIDTH = 8,
    parameter SHIFT_DIRECTION = "LEFT" // "LEFT" or "RIGHT"
)(
    input wire sclr,          // Synchronous clear
    input wire sset,          // Synchronous set
    input wire shiftin,       // Serial shift data input
    input wire load,          // Synchronous parallel load
    input wire [SHIFT_WIDTH-1:0] data, // Data input
    input wire clock,         // Clock input
    input wire enable,        // Clock enable
    input wire aclr,          // Asynchronous clear
    input wire aset,          // Asynchronous set
    output reg shiftout,       // Serial shift data output
    output reg [SHIFT_WIDTH-1:0] q // Data output
);

always @(posedge clock or posedge aclr or posedge aset) begin
    if (aclr) begin
        q <= 0;
    end else if (aset) begin
        q <= LOAD_AVALUE;
    end else if (enable) begin
        if (sclr) begin
            q <= 0;
        end else if (sset) begin
            q <= LOAD_SVALUE;
        end else if (load) begin
            q <= data;
        end else begin
            if (SHIFT_DIRECTION == "LEFT") begin
                shiftout <= q[SHIFT_WIDTH-1];
                // shiftout gets the leftmost bit of q
                q <= {q[SHIFT_WIDTH-2:0], shiftin};
                // Shift left and append shiftin to the rightmost bit
            end else if (SHIFT_DIRECTION == "RIGHT") begin
                shiftout <= q[0]; // shiftout gets the rightmost bit of q
                q <= {shiftin, q[SHIFT_WIDTH-1:1]};
                // Shift right and append shiftin to the leftmost bit
            end
        end
    end
end
end
endmodule
```

```

module param_shift_register_tb;
    // Declare testbench signals
    reg sclr;
    reg sset;
    reg shiftin;
    reg load;
    reg [7:0] data; // SHIFT_WIDTH = 8
    reg clock;
    reg enable;
    reg aclr;
    reg aset;
    wire shiftout;
    wire [7:0] q;

    // Instantiate the parameterized shift register
    param_shift_register #(
        .LOAD_AVALUE(2),           // LOAD_AVALUE = 2
        .LOAD_SVALUE(4),           // LOAD_SVALUE = 4
        .SHIFT_DIRECTION("LEFT"), // SHIFT_DIRECTION = "LEFT"
        .SHIFT_WIDTH(8)            // SHIFT_WIDTH = 8
    ) uut (
        .sclr(sclr),
        .sset(sset),
        .shiftin(shiftin),
        .load(load),
        .data(data),
        .clock(clock),
        .enable(enable),
        .aclr(aclr),
        .aset(aset),
        .shiftout(shiftout),
        .q(q)
    );

    // Clock generation: 10 time unit period
    always begin
        #5 clock = ~clock; // Generate a clock with a period of 10 time units
    end

    // Task to verify expected behavior and output q
    task verify_q(input [7:0] expected_q);
        begin
            if (q == expected_q)
                $display("TEST PASSED: Expected q = %b, Actual q = %b", expected_q, q);
            else
                $display("TEST FAILED: Expected q = %b, Actual q = %b", expected_q, q);
        end
    endtask
endtask

```

```

// Stimulus process: Generate test cases
initial begin
    // Initialize signals
    clock = 0;
    sclr = 0;
    sset = 0;
    shiftin = 0;
    load = 0;
    data = 8'b00000000;
    enable = 1;
    aclr = 0;
    aset = 0;

    // Test 2.1: Verify Asynchronous Clear (aclr)
    aclr = 1; // Assert aclr
    aset = 0; // Deassert aset
    #10; // Wait a few time units
    verify_q(8'b00000000); // q should be cleared

    // Test 2.2: Verify Asynchronous Set (aset)
    aclr = 0; // Deassert aclr
    aset = 1; // Assert aset
    #10; // Wait a few time units
    verify_q(8'b00000010); // q should be loaded with LOAD_AVALUE (2)

    // Test 2.3: Verify Synchronous Clear (sclr)
    aclr = 0; // Deassert aclr
    aset = 0; // Deassert aset
    sclr = 1; // Assert sclr
    sset = 0; // Deassert sset
    #10; // Wait a few time units
    verify_q(8'b00000000); // q should be cleared due to sclr

    // Test 2.4: Verify Synchronous Set (sset)
    sclr = 0; // Deassert sclr
    sset = 1; // Assert sset
    #10; // Wait a few time units
    verify_q(8'b00000100); // q should be loaded with LOAD_SVALUE (4)

    // Test 2.5: Verify Load Functionality
    sclr = 0; // Deassert sclr
    sset = 0; // Deassert sset
    load = 1; // Assert load
    data = 8'b11011011; // Set input data
    #10; // Wait a few time units
    verify_q(8'b11011011); // q should be loaded with the data value

```





```

# At time          0: q = 00000000, shiftout = x
# TEST PASSED: Expected q = 00000000, Actual q = 00000000
# At time          10: q = 00000010, shiftout = x
# TEST PASSED: Expected q = 00000010, Actual q = 00000010
# At time          25: q = 00000000, shiftout = x
# TEST PASSED: Expected q = 00000000, Actual q = 00000000
# At time          35: q = 00000100, shiftout = x
# TEST PASSED: Expected q = 00000100, Actual q = 00000100
# At time          45: q = 11011011, shiftout = x
# TEST PASSED: Expected q = 11011011, Actual q = 11011011
# At time          55: q = 10110111, shiftout = 1
# TEST PASSED: Expected q = 10110111, Actual q = 10110111
# At time          65: q = 01101111, shiftout = 1
# TEST PASSED: Expected q = 01101111, Actual q = 01101111
# At time          75: q = 11011111, shiftout = 0
# At time          85: q = 10111111, shiftout = 1
# At time          90: q = 00000000, shiftout = 1
# At time         180: q = 00000010, shiftout = 1
# At time         215: q = 00000000, shiftout = 1

```

5.

```

module SLE (
    input wire D,          // Data input
    input wire CLK,        // Clock input
    input wire EN,         // Enable
    input wire ALn,        // Asynchronous Load (Active Low)
    input wire ADn,        // Asynchronous Data (Active Low)
    input wire SLn,        // Synchronous Load (Active Low)
    input wire SD,         // Synchronous Data
    input wire LAT,        // Latch Enable
    output reg Q           // Output
);

// Always block for asynchronous operations (Asynchronous Load)
always @(posedge CLK or negedge ALn) begin
    if (!ALn) begin
        Q <= ADn; // Asynchronous load when ALn is low
    end
    else if (EN) begin
        if (!SLn) begin
            Q <= SD; // Synchronous load when SLn is low
        end
        else if (!LAT) begin
            Q <= D; // Flip-Flop Mode (LAT=0)
        end
    end
end

```

```

        end
    end

    // Always block for latch behavior (LAT=1)
    always @(*) begin
        if (LAT) begin
            Q = D; // Latch Mode (Transparent when LAT=1)
        end
    end

endmodule

module SLE_tb;
    // Testbench Signals
    reg D, CLK, EN, ALn, ADn, SLn, SD, LAT;
    wire Q;

    // Instantiate the DUT (Device Under Test)
    SLE uut (
        .D(D),
        .CLK(CLK),
        .EN(EN),
        .ALn(ALn),
        .ADn(ADn),
        .SLn(SLn),
        .SD(SD),
        .LAT(LAT),
        .Q(Q)
    );

    // Clock Generation (50% Duty Cycle)
    initial begin
        CLK = 0;
        forever #5 CLK = ~CLK; // Toggle clock every 5ns
    end

    // Test Sequence
    initial begin
        // Step 1: Activate ALn (Set to 0)
        ALn = 0;
        ADn = $random; // Random asynchronous data
        #10;
        $display("TEST: ALn Activated | Expected Q = %b, Actual Q = %b", ADn, Q);

        // Step 2: Deactivate ALn (Set to 1)
        ALn = 1;
        #10;
    end
endmodule

```


```

// Step 3: Flip-Flop Mode (LAT = 0)
LAT = 0;
repeat (10) begin
    {D, EN, SLn, SD} = $random; // Randomize inputs
    #10;
    $display("Flip-Flop Mode | D = %b, EN = %b, SLn = %b, SD = %b, Q =
%b", D, EN, SLn, SD, Q);
end

// Step 4: Latch Mode (LAT = 1)
LAT = 1;
repeat (10) begin
    {D, EN, SLn, SD} = $random; // Randomize inputs
    #10;
    $display("Latch Mode | D = %b, EN = %b, SLn = %b, SD = %b, Q = %b",
D, EN, SLn, SD, Q);
end

$finish;
end
endmodule

```

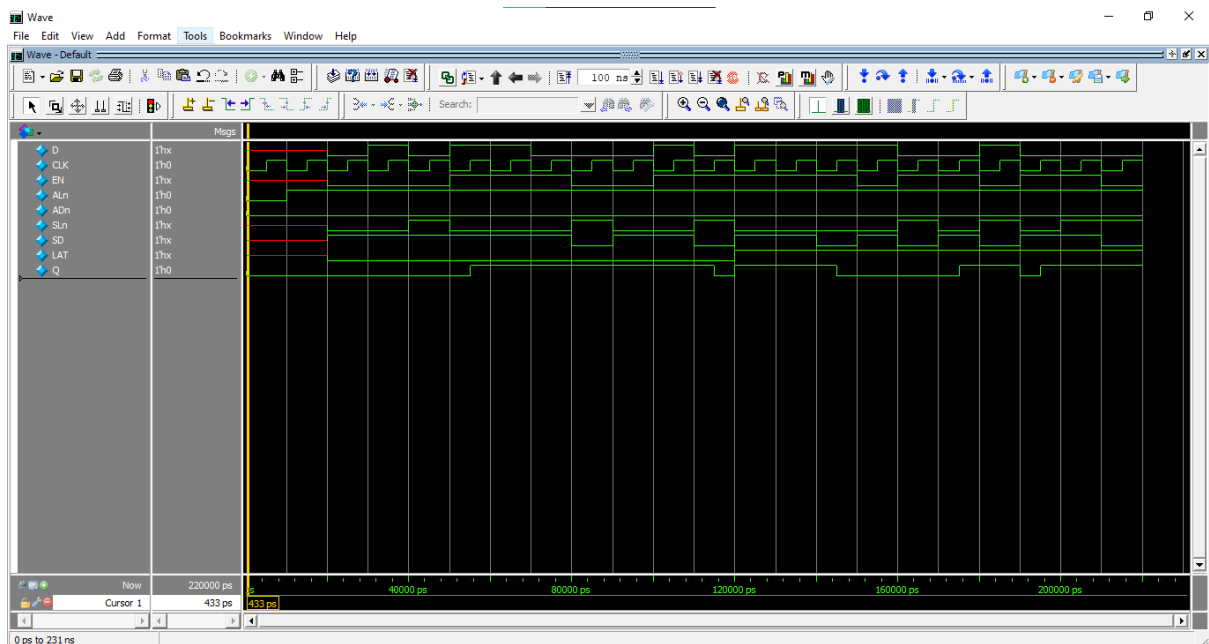

```

# TEST: ALn Activated | Expected Q = 0, Actual Q = 0
# Flip-Flop Mode | D = 0, EN = 0, SLn = 0, SD = 1, Q = 0
# Flip-Flop Mode | D = 1, EN = 0, SLn = 0, SD = 1, Q = 0
# Flip-Flop Mode | D = 0, EN = 0, SLn = 1, SD = 1, Q = 0
# Flip-Flop Mode | D = 1, EN = 1, SLn = 0, SD = 1, Q = 1
# Flip-Flop Mode | D = 1, EN = 1, SLn = 0, SD = 1, Q = 1
# Flip-Flop Mode | D = 0, EN = 1, SLn = 0, SD = 1, Q = 1
# Flip-Flop Mode | D = 0, EN = 0, SLn = 1, SD = 0, Q = 1
# Flip-Flop Mode | D = 0, EN = 0, SLn = 0, SD = 1, Q = 1
# Flip-Flop Mode | D = 1, EN = 1, SLn = 0, SD = 1, Q = 1
# Flip-Flop Mode | D = 0, EN = 1, SLn = 1, SD = 0, Q = 0

# Latch Mode | D = 1, EN = 1, SLn = 0, SD = 1, Q = 1
# Latch Mode | D = 1, EN = 1, SLn = 0, SD = 1, Q = 1
# Latch Mode | D = 1, EN = 1, SLn = 0, SD = 0, Q = 0
# Latch Mode | D = 1, EN = 0, SLn = 0, SD = 1, Q = 0
# Latch Mode | D = 0, EN = 1, SLn = 1, SD = 0, Q = 0
# Latch Mode | D = 0, EN = 1, SLn = 0, SD = 1, Q = 1
# Latch Mode | D = 1, EN = 0, SLn = 1, SD = 0, Q = 1
# Latch Mode | D = 0, EN = 1, SLn = 0, SD = 1, Q = 1
# Latch Mode | D = 0, EN = 1, SLn = 1, SD = 1, Q = 1
# Latch Mode | D = 0, EN = 0, SLn = 1, SD = 0, Q = 1

```